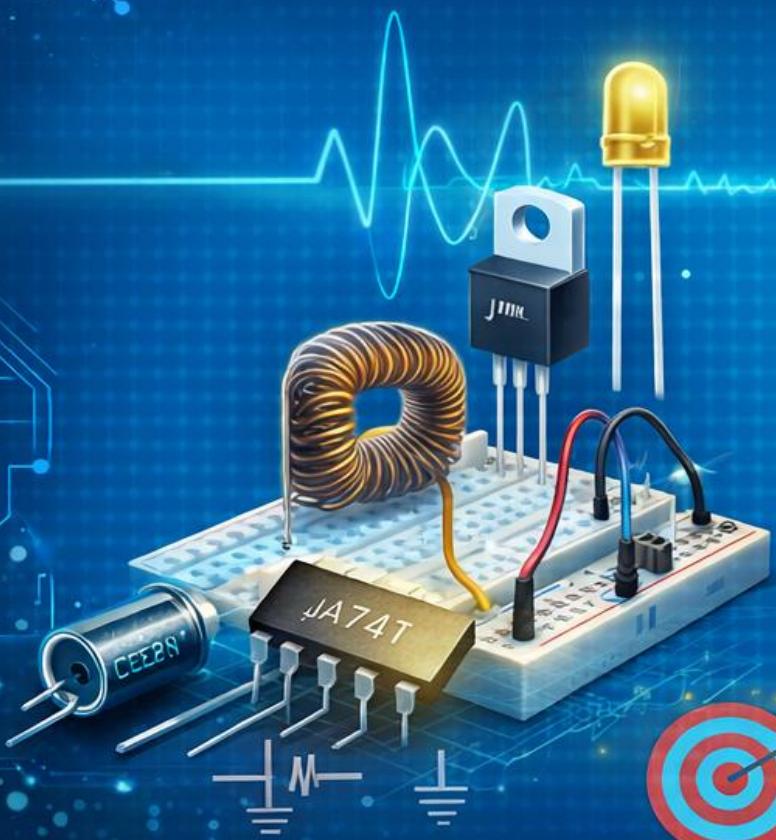


# ANALOG ELECTRONICS

- PN JUNCTION DIODES
- TRANSISTORS (BJT, FET, MOSFET)
- AMPLIFIERS (OP-AMP)
- OSCILLATORS

Your Study Partner In Success!



**CAREER FI**  
INDIA

## Analog Electronics – Short & Clear Overview

Analog Electronics deals with electronic circuits in which signals vary continuously with time (voltage/current), unlike digital electronics which uses discrete levels.

### 1. Explain the DC load line analysis of a PN junction diode.

DC load line analysis is a graphical method used to determine the operating point (Q-point) of a PN junction diode when it is connected in a DC circuit. Consider a diode connected in series with a resistor and a DC supply voltage. By applying Kirchhoff's Voltage Law (KVL) to the circuit, the relation between diode current and diode voltage can be written as:

$$V = IR + V_D$$

where  $V$  is the supply voltage,  $R$  is the series resistance, and  $V_D$  is the diode voltage. This equation represents a straight line on the diode V-I characteristics and is called the **DC load line**.

The load line intersects the current axis at  $I = V/R$  (when  $V_D = 0$ ) and the voltage axis at  $V_D = V$  (when  $I = 0$ ). The point where the load line intersects the diode's V-I characteristic curve gives the operating point or Q-point of the diode. This Q-point indicates the actual diode current and voltage under given circuit conditions. DC load line analysis is important because it helps predict diode behavior in rectifiers and electronic circuits under different biasing conditions.

### 2. Explain the working of a clumper and its types.

A clumper is an electronic circuit that shifts the entire waveform of an AC signal either upward or downward without changing its shape. The main purpose of a clumper is to add a DC component to an AC signal so that the signal is "clamped" to a desired voltage level. A clumper circuit typically consists of a diode, a capacitor, and a resistor.

During operation, the capacitor charges during one half cycle of the input signal through the diode. In the next half cycle, the diode becomes reverse biased, and the capacitor retains its charge. This stored charge adds or subtracts a DC level from the input signal, resulting in a shifted output waveform. The resistor provides a discharge path and ensures proper operation of the circuit.

There are mainly **two types of clumpers**:

- **Positive clumper:** It shifts the input waveform upward, clamping the negative peak to the reference level (usually zero).
- **Negative clumper:** It shifts the input waveform downward, clamping the positive peak to the reference level.

Clumpers are widely used in television receivers, signal restoration circuits, and voltage level shifting applications.

### 3. Write the properties of an operational amplifier.

An operational amplifier (op-amp) is a high-gain DC-coupled electronic amplifier with differential inputs and a single output. One of the most important properties of an ideal operational amplifier is **very high open-loop voltage gain**, which allows it to amplify very small input signals. Another key property is **very high input impedance**, ensuring that it draws negligible current from the input source.

An op-amp also has **very low output impedance**, which enables it to drive loads efficiently without significant voltage drop. Ideally, an operational amplifier has **infinite bandwidth**, meaning it can amplify signals of any frequency without attenuation. Additionally, an ideal op-amp has **zero offset voltage**, so the output is exactly zero when both inputs are zero. In practical op-amps, these ideal characteristics are approximated but not fully achieved. Due to their versatile properties, operational amplifiers are extensively used in amplifiers, filters, oscillators, integrators, and control systems.

### 4. Explain multivibrator and its types.

A multivibrator is an electronic circuit that generates non-sinusoidal waveforms such as square or rectangular waves. It uses active devices like transistors or operational amplifiers along with resistors and capacitors. Multivibrators are commonly used as timing circuits, pulse generators, and memory elements in digital electronics.

There are **three main types of multivibrators** based on their stability states. The **astable multivibrator** has no stable state and continuously switches between two states, producing a square wave output. The **monostable multivibrator** has one stable and one unstable state; when triggered, it produces a single output pulse and then returns to its stable state. The **bistable multivibrator** has two stable states and remains in one state until an external trigger forces it to switch to the other. Multivibrators play a crucial role in digital circuits, clock generation, flip-flops, counters, and timing applications.

### 1. Explain the working of a rectifier and its types

A rectifier is an electronic circuit that converts alternating current (AC) into direct current (DC). Rectification is essential because most electronic devices require DC for their operation. Rectifiers mainly use PN junction diodes due to their unidirectional conduction property.

**Working of a Rectifier**

When an AC voltage is applied to a diode-based circuit, the diode conducts during one half cycle and blocks during the opposite half cycle. As a result, current flows in only one direction through the load. The output obtained is pulsating DC, which can later be smoothed using filters.

#### Types of Rectifier

##### 1. Half-Wave Rectifier:

It uses a single diode. During the positive half cycle, the diode conducts and current flows through the load. During the negative half cycle, the diode is reverse biased and no current flows. The output contains large ripples and low efficiency.


##### 2. Full-Wave Rectifier:

It converts both halves of the AC input into DC.

- **Center-tapped full-wave rectifier** uses two diodes and a center-tapped transformer.


- **Bridge rectifier** uses four diodes and does not require a center-tapped transformer.

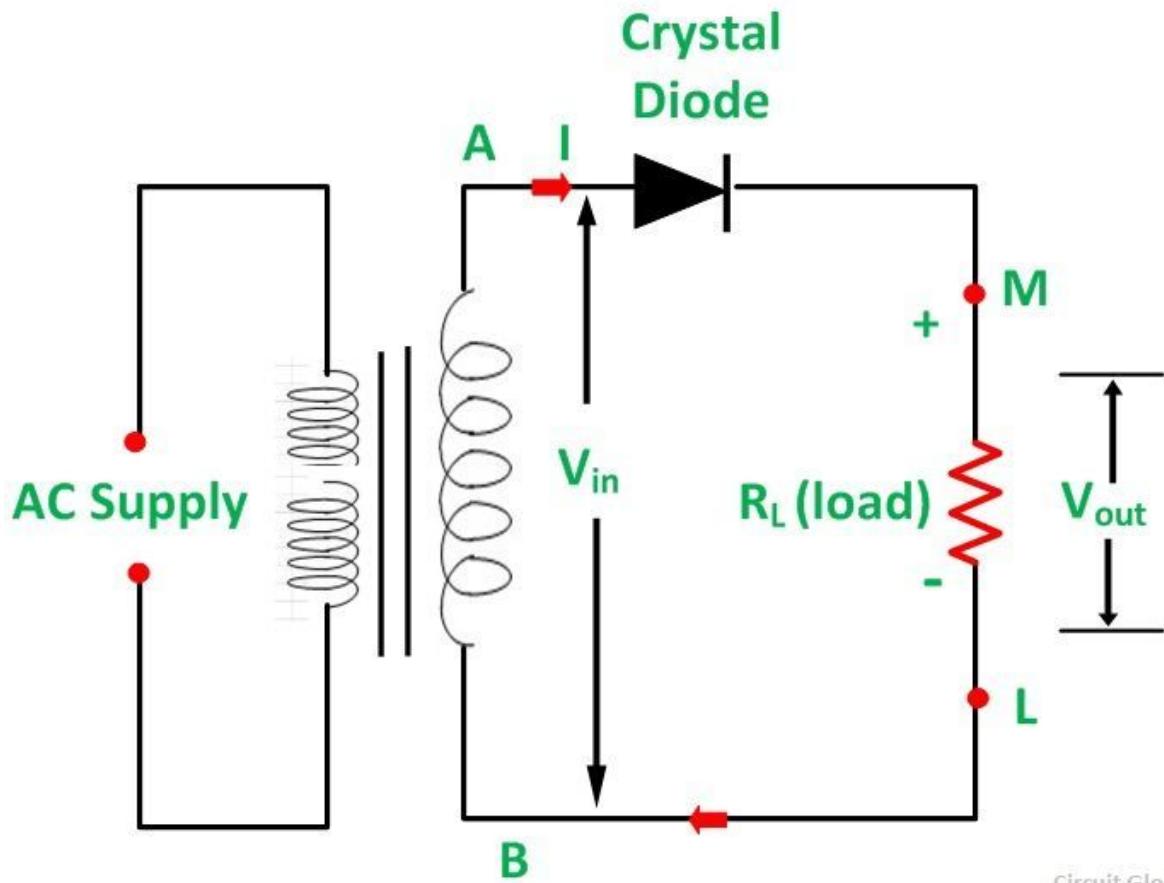Full-wave rectifiers have higher efficiency, lower ripple factor, and better output than half-wave rectifiers.



Circuit Globe

# Full Wave Rectifier

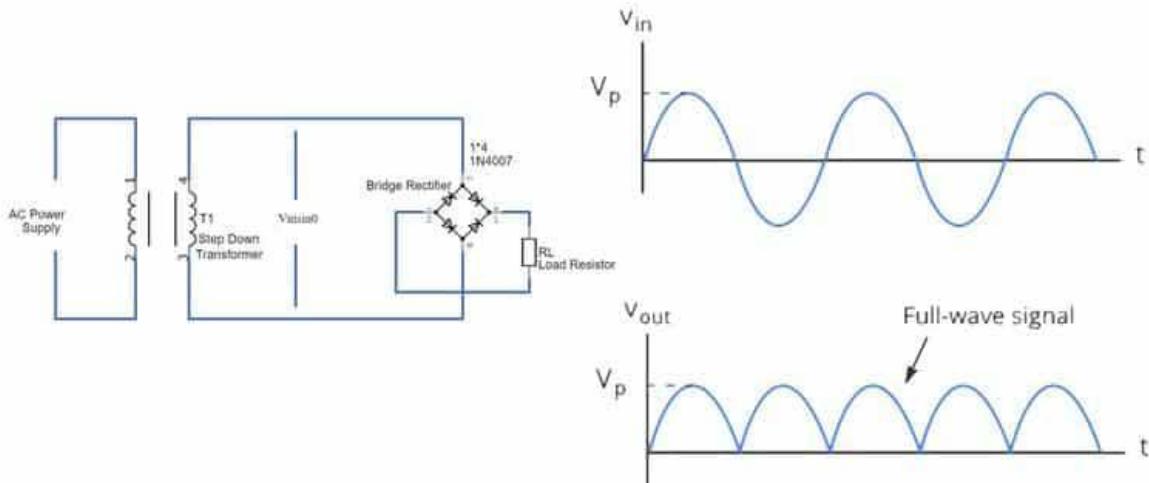

## 2. Explain the working of a clipper and its types


A clipper is an electronic circuit used to remove or “clip” a portion of an input waveform without affecting the remaining part. Clippers are mainly used for wave shaping and overvoltage protection.



### Working of a Clipper

A clipper circuit consists of a diode, resistor, and sometimes a DC voltage source. When the input signal exceeds a certain reference level, the diode conducts and clips the signal beyond that level. When the signal is within the limit, the diode remains non-conducting, and the output follows the input.

### Types of Clippers

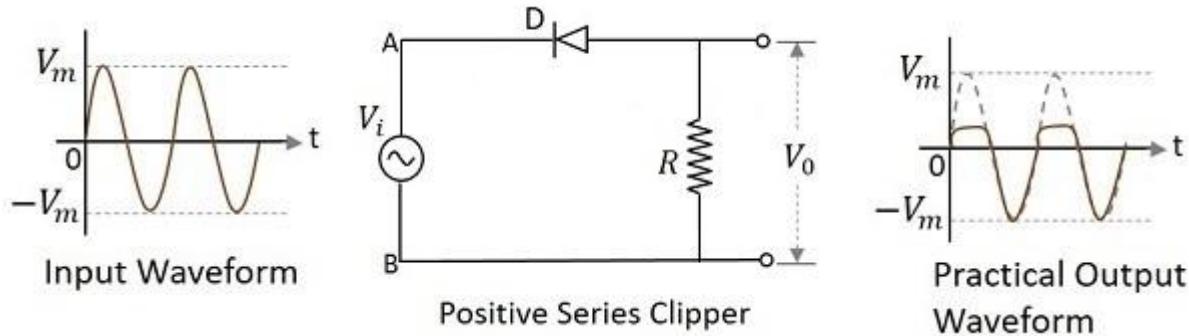1. **Positive Clipper:** Removes the positive portion of the input waveform.
2. **Negative Clipper:** Removes the negative portion of the input waveform.
3. **Series Clipper:** Diode is connected in series with the load.
4. **Shunt Clipper:** Diode is connected in parallel with the load.
5. **Biased Clipper:** Uses a DC source to clip at a specific voltage level other than zero.



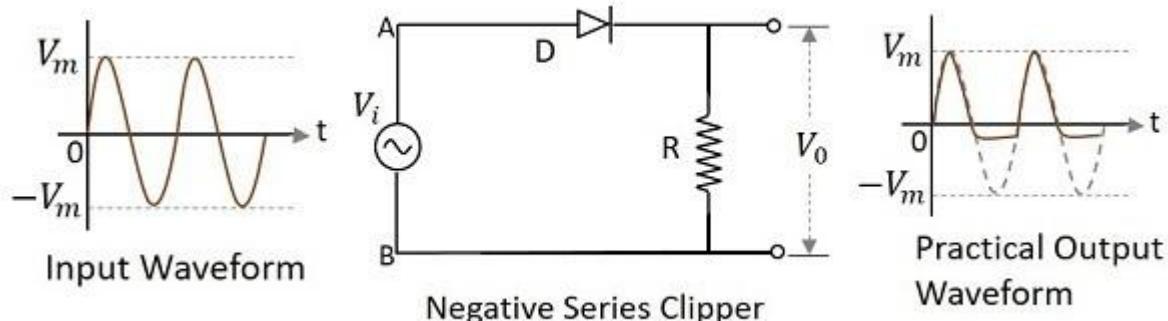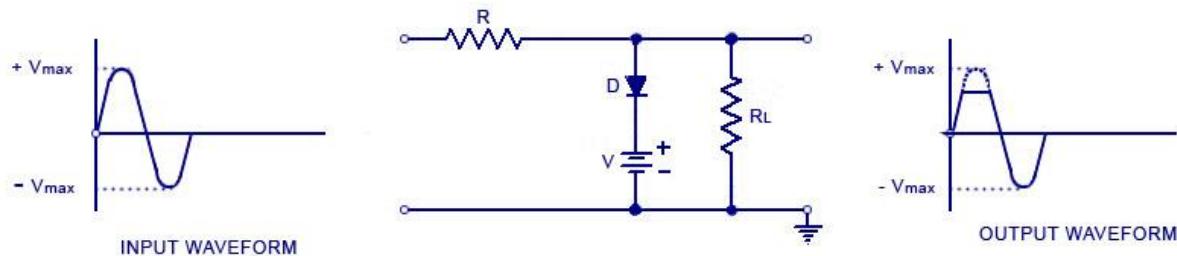
**BIASED POSITIVE CLIPPER**

[www.CircuitsToday.com](http://www.CircuitsToday.com)

### 3. Explain the common base connection of a BJT with circuit diagram, derivation of alpha, input and output characteristics

In the **common base (CB) configuration**, the base terminal is common to both input and output circuits. The input is applied between emitter and base, while the output is taken from collector and base.

#### Working of Common Base Configuration

In this configuration, the emitter-base junction is forward biased and the collector-base junction is reverse biased. Majority carriers injected from the emitter cross the thin base region and are collected by the collector, resulting in collector current.

#### Derivation of Current Gain ( $\alpha$ )

$$\alpha = \frac{I_C}{I_E}$$


Since collector current is slightly less than emitter current, the value of  $\alpha$  is less than unity, typically ranging from 0.95 to 0.99.

#### Input Characteristics

The input characteristics represent the variation of emitter current with emitter-base voltage at constant collector-base voltage. The curve resembles that of a forward-biased diode.


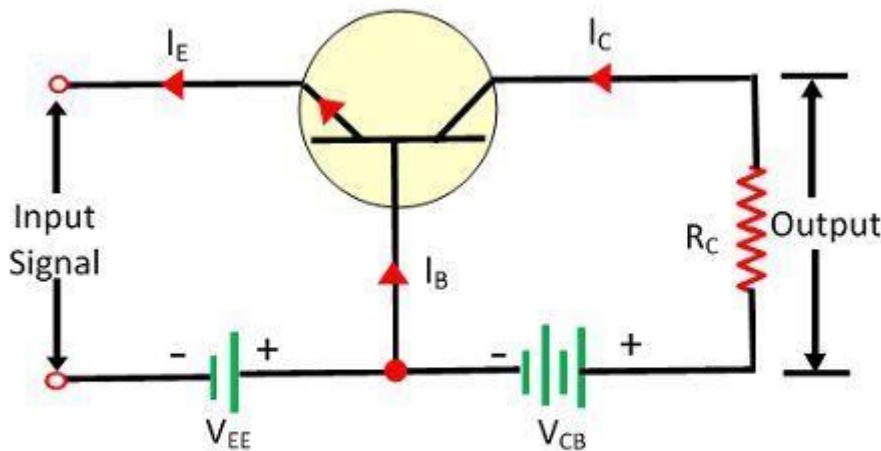
#### Output Characteristics

The output characteristics show the relationship between collector current and collector-base voltage at constant emitter current. Collector current remains almost constant, indicating good current stability.



### Common Base Connection of NPN Transistor

Circuit Globe

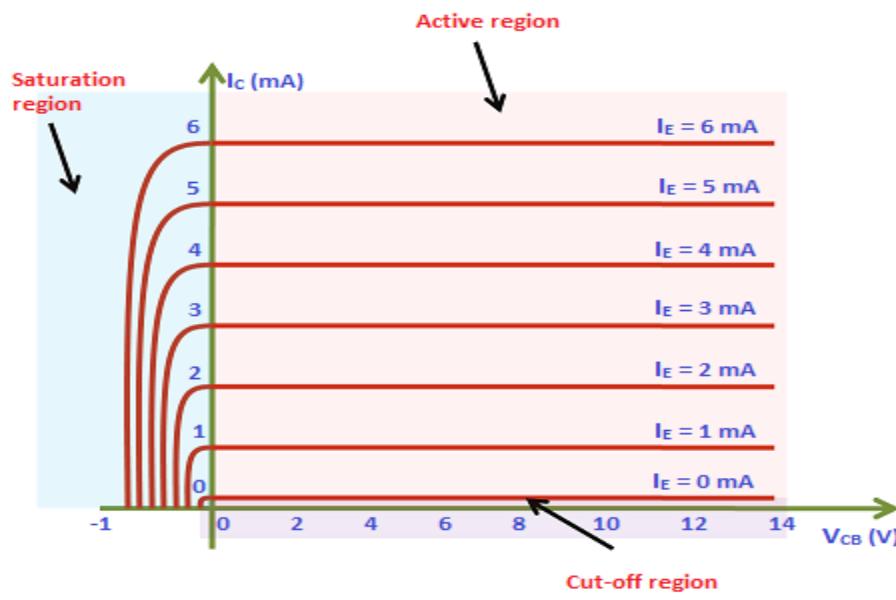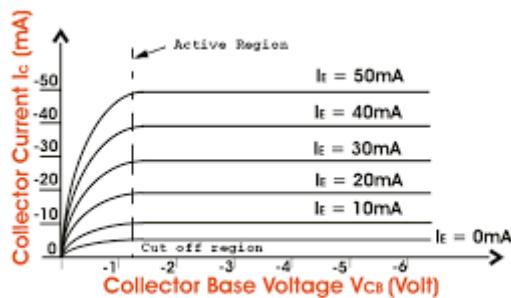

O/P characteristics CB configuration

4. Explain the common emitter connection of a BJT with circuit diagram, derivation of beta, input and output characteristics

In the **common emitter (CE) configuration**, the emitter terminal is common to both input and output. The input is applied between base and emitter, and the output is taken between collector and emitter.

### Working of Common Emitter Configuration

The base-emitter junction is forward biased and the collector-emitter junction is reverse biased. A small base current controls a much larger collector current, resulting in high current and voltage gain.

### Derivation of Current Gain ( $\beta$ )

$$\beta = \frac{I_C}{I_B}$$



The value of  $\beta$  is high, typically ranging from 20 to 300, making CE configuration widely used for amplification.

### Input Characteristics

The input characteristics show the variation of base current with base-emitter voltage at constant collector-emitter voltage. It resembles a forward-biased diode characteristic.
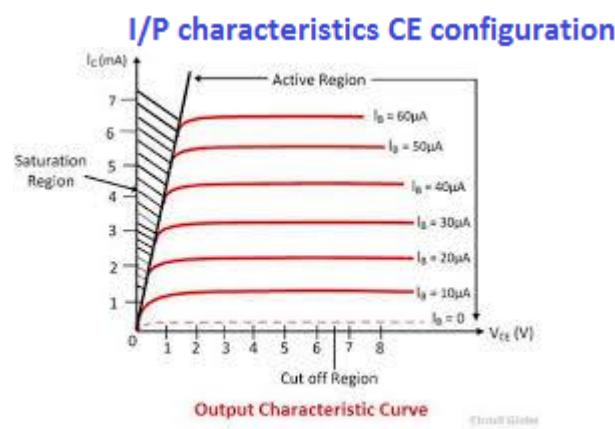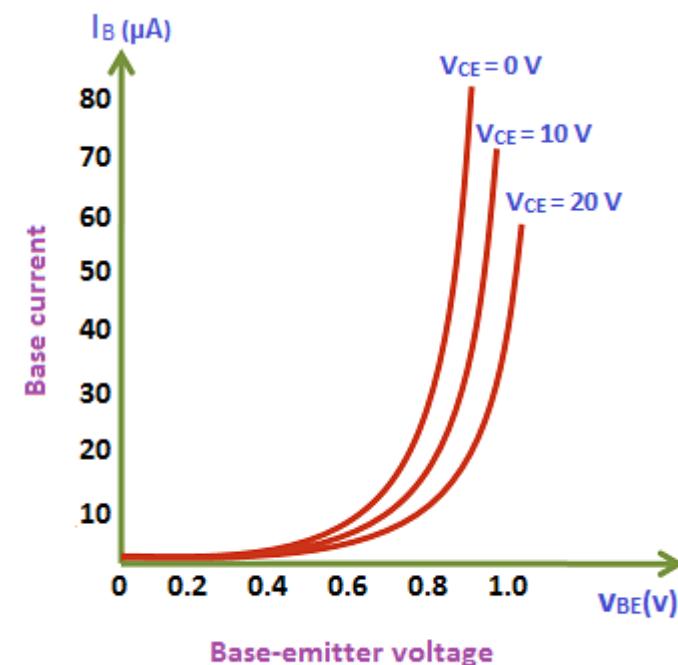
### Output Characteristics

The output characteristics show the variation of collector current with collector-emitter voltage at constant base current. The curves show cutoff, active, and saturation regions.



## 5. Explain the construction, working and principle of a JFET

A Junction Field Effect Transistor (JFET) is a unipolar, voltage-controlled device in which current conduction occurs due to majority carriers only.

### Construction

A JFET consists of a semiconductor channel (n-type or p-type) with two terminals called source and drain. Two heavily doped regions form the gate, creating a PN junction with the channel.

### Principle of Operation


The operation of JFET is based on the control of channel width by the gate-to-source voltage. When reverse bias is applied to the gate, the depletion region widens and reduces the channel width.

### Working


As gate voltage increases in reverse bias, the drain current decreases. At a certain gate voltage, the channel becomes completely pinched off, and drain current becomes constant.




**N-Channel JFET**

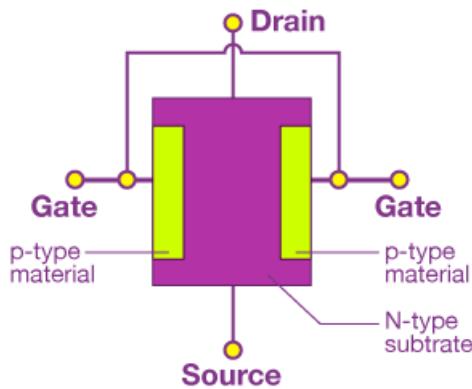

**P-Channel JFET**

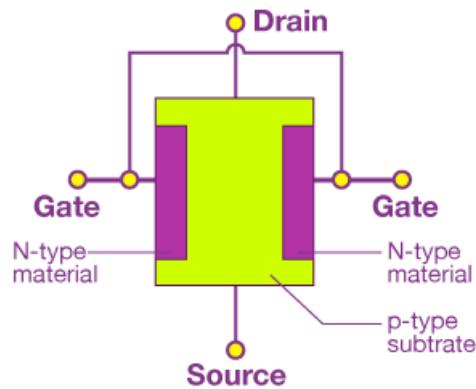

## N-Channel JFET Characteristics Curve

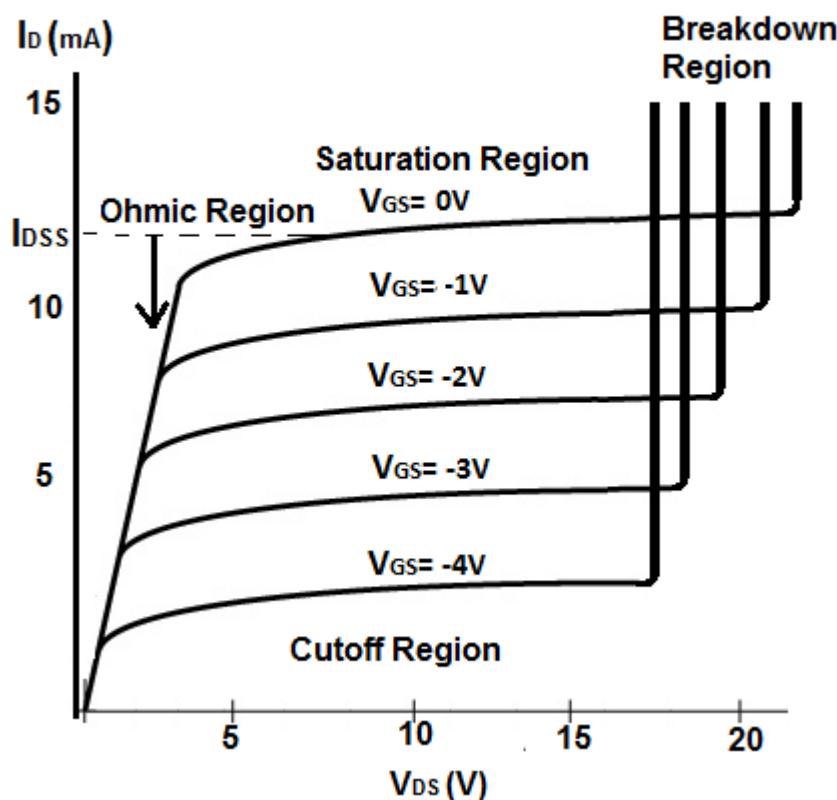

### 6. Explain MOSFET and its types

A Metal Oxide Semiconductor Field Effect Transistor (MOSFET) is a voltage-controlled semiconductor device widely used in digital and power electronics.


#### Working Principle

In a MOSFET, the gate terminal is insulated from the channel by a thin oxide layer. When a voltage is applied to the gate, it creates an electric field that controls the conductivity of the channel.


#### Types of MOSFET

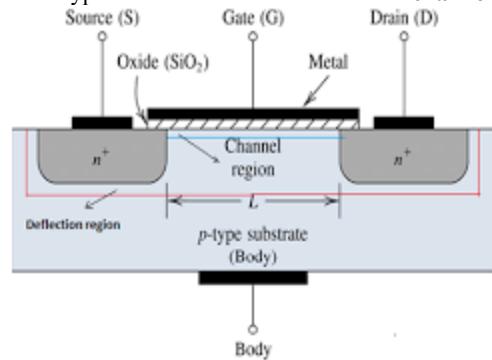
1. **Enhancement Type MOSFET:** Channel is induced only when gate voltage is applied.
2. **Depletion Type MOSFET:** Channel exists even at zero gate voltage.

Each type can further be classified into **n-channel** and **p-channel** MOSFETs.



## Enhancement and Depletion MOSFET

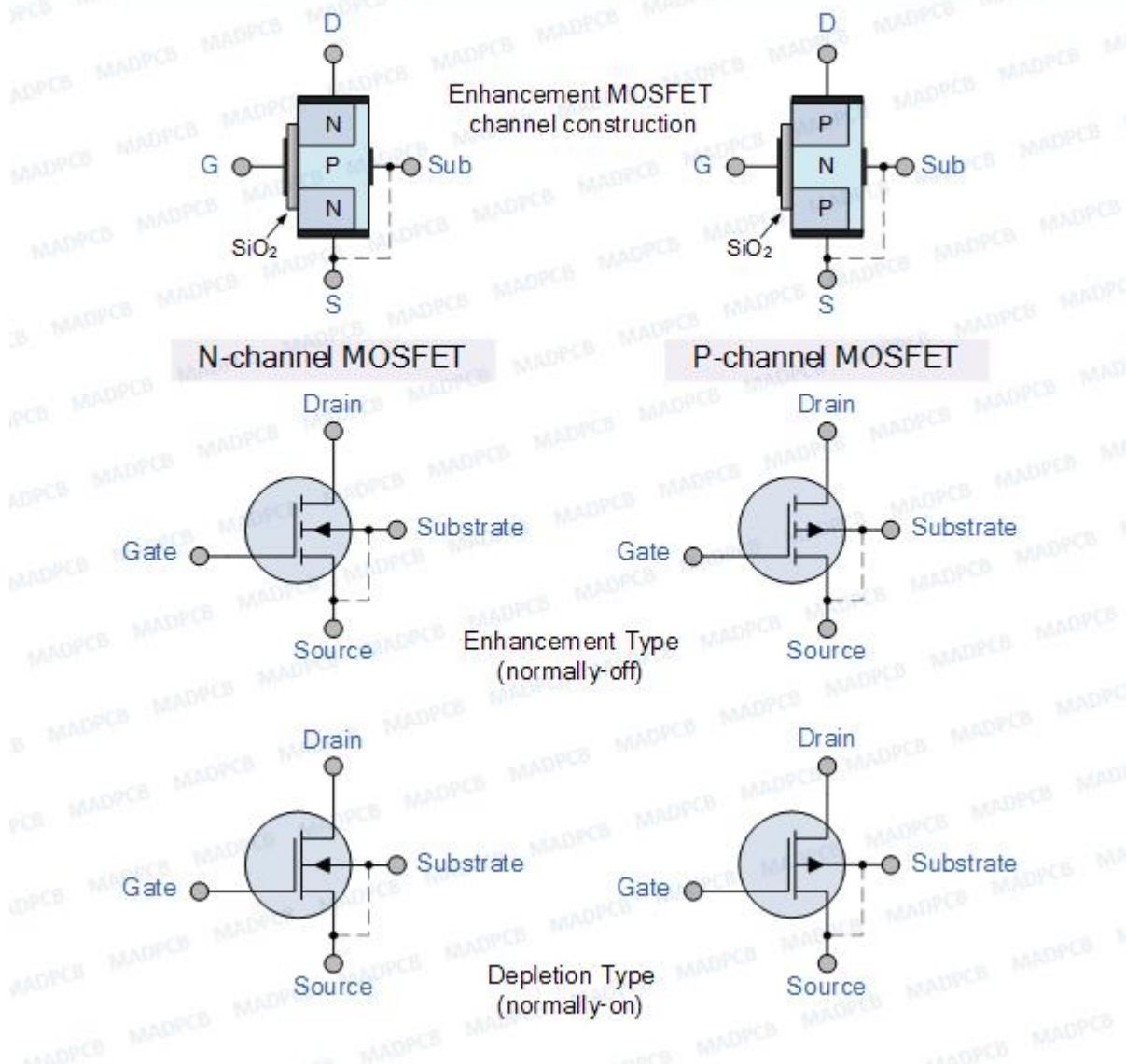

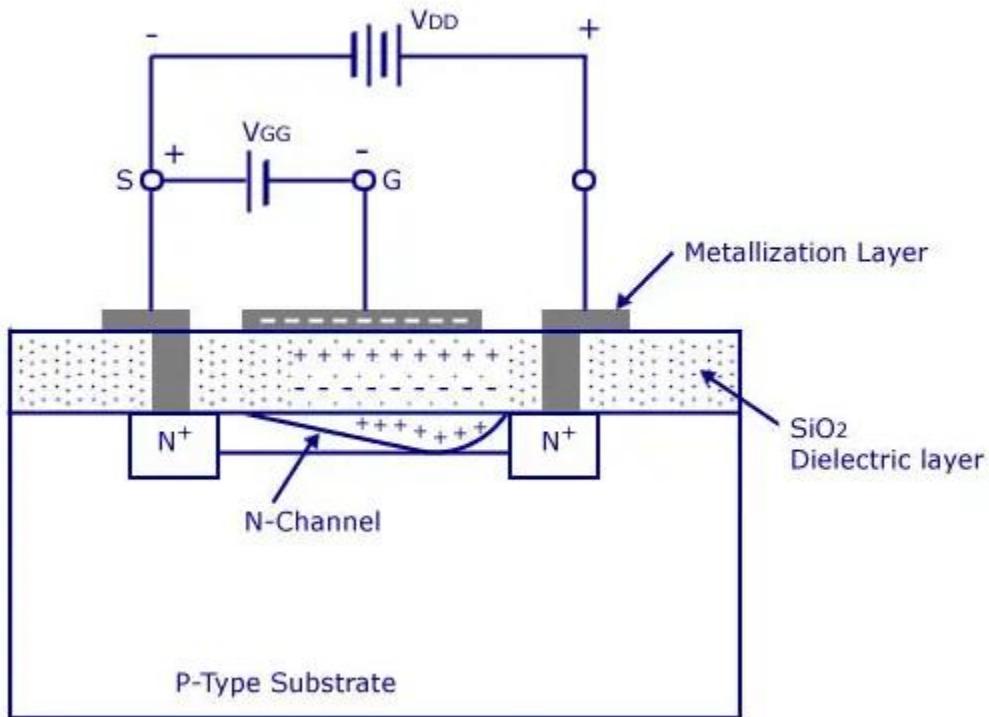

#### 7. Explain Hartley Oscillator

A Hartley oscillator is an LC oscillator that uses a tapped inductor or two inductors and a capacitor to generate high-frequency sinusoidal oscillations.



##### Working

The oscillator uses positive feedback obtained through inductive coupling. When power is supplied, oscillations are initiated due to noise. The tank circuit determines the frequency of oscillation.
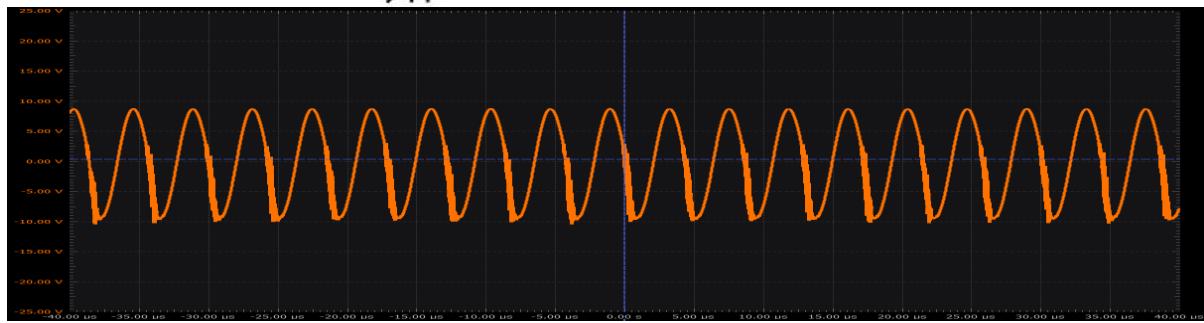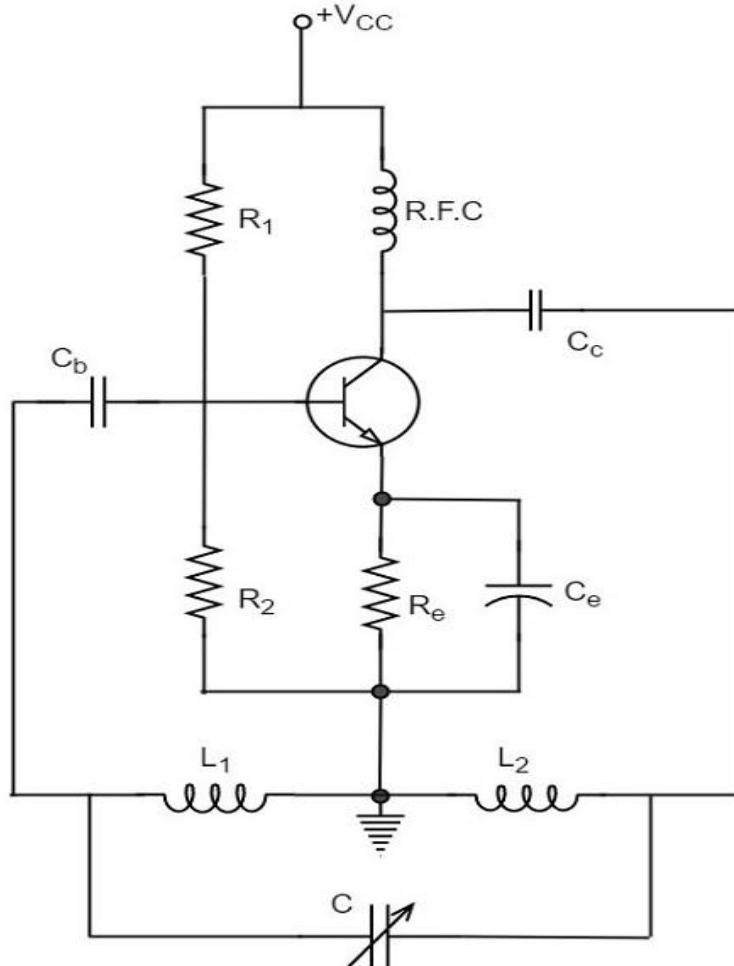
##### Frequency of Oscillation

$$f = \frac{1}{2\pi\sqrt{(L_1 + L_2)C}}$$

Hartley oscillators are widely used in radio frequency generators and receivers.



#### 8. Explain Colpitt's Oscillator

A Colpitt's oscillator is an LC oscillator that uses two capacitors and one inductor in the tank circuit.

##### Working

The two capacitors form a capacitive voltage divider that provides the required feedback. The oscillations are sustained due to positive feedback and energy exchange between the inductor and capacitors.

##### Frequency of Oscillation

$$f = \frac{1}{2\pi \sqrt{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}$$

Colpitt's oscillator is preferred for high-frequency applications due to its better stability.

